

Total No. of Questions—8]

[Total No. of Printed Pages—5

Seat No.	
-------------	--

[5459]-157

S.E. (Electrical Engg.) (Second Semester) EXAMINATION, 2018

NETWORK ANALYSIS

(2015 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Answer Q. Nos. 1 or 2, Q. Nos. 3 or 4, Q. Nos. 5 or 6, Q. Nos. 7 or 8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.

(iv) Assume suitable data, if necessary.

1. (a) Using mesh analysis, find the magnitude of dependent source. [7]

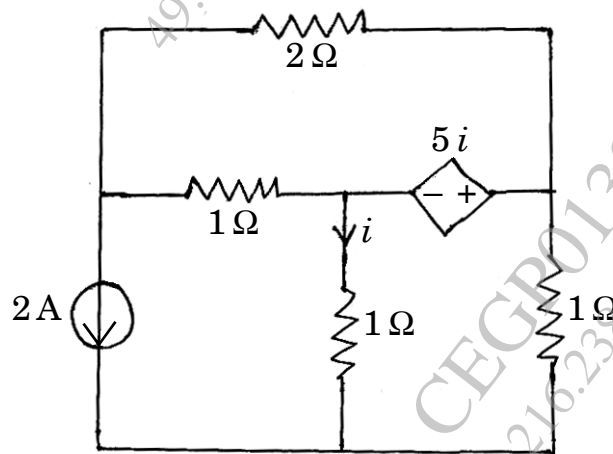


Fig. 1

P.T.O.

- (b) Find Norton's equivalent circuit for the network shown in Fig. 2 : [6]

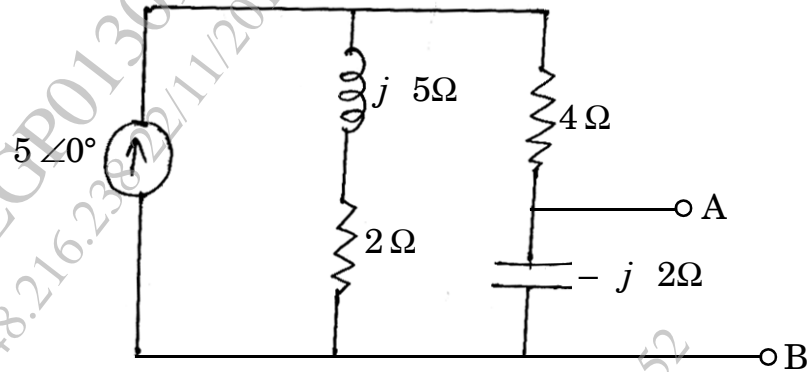


Fig. 2

Or

2. (a) State and explain the concept of duality with suitable example. [6]
- (b) Using superposition theorem, calculate current ' i ' for the circuit shown in Fig. 3 : [7]

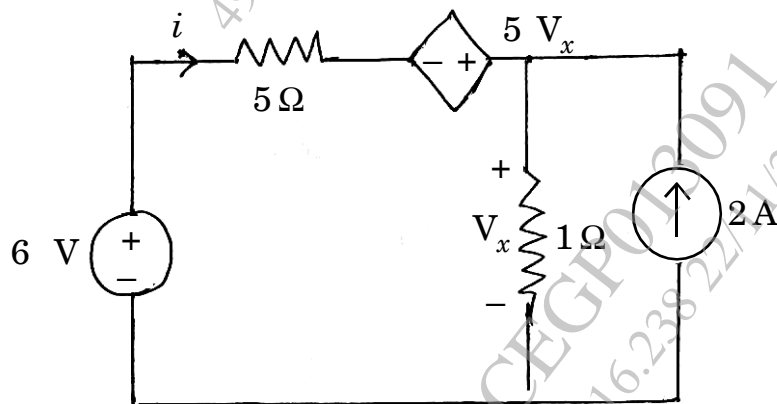


Fig. 3

3. (a) Using classical theory, find voltage across inductor at time $t = 2$, sec, after switch is opened : [6]

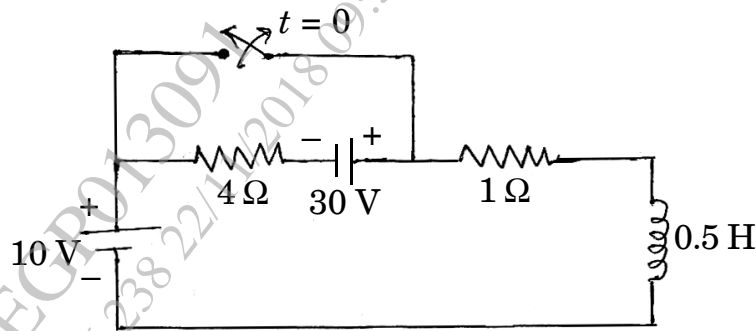


Fig. 4

- (b) For the circuit shown in Fig. 5 solve for $i(t)$ using Laplace transform with switch 'k' closed at $t = 0$: [6]

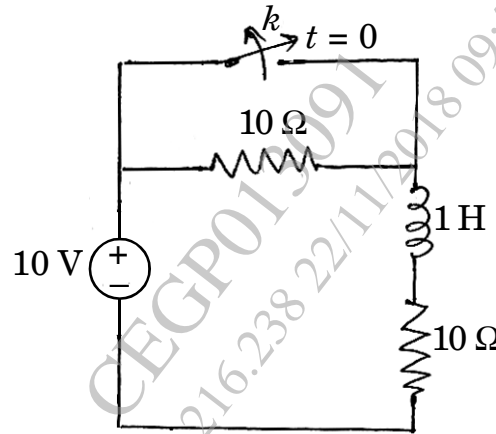


Fig. 5

Or

4. (a) R-L-C circuit is excited by D.C. voltage source. Find current $i(t)$ using conventional method. The switch is closed at time $t = 0$. [6]

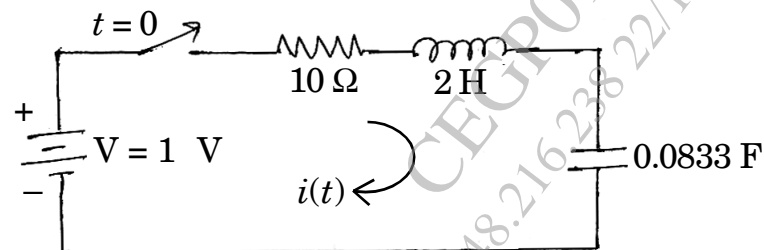


Fig. 6

- (b) In the circuit shown in Fig. 7, the switch is moved to position 2 at time $t = 0$, find the expression of current for time $t > 0$, using Laplace transform : [6]

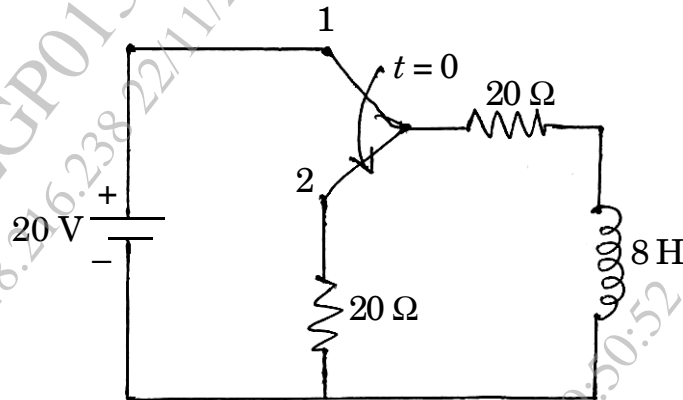


Fig. 7

5. (a) Obtain 'Y' parameters in terms of transmission parameters. [6]
- (b) Draw poles and zeros plot in the S plane of the driving point impedance function for the network shown in Fig. 8 : [7]

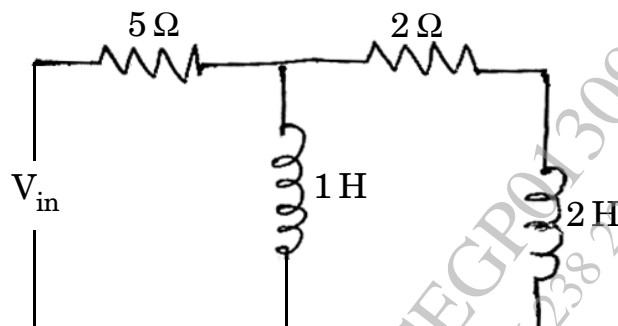


Fig. 8

Or

6. (a) Find transmission parameter for the network shown in Fig. 9 : [7]

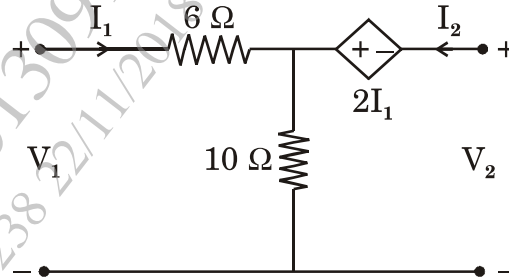


Fig. 9

- (b) Explain the necessary conditions for transfer function. [6]
7. (a) Derive an expression for characteristic impedance (Z_{OT} and $Z_{O\pi}$), attenuation constant (α) and phase constant (β) of constant k high pass filter from symmetrical network. [6]
- (b) Design a prototype low pass filter (π and T section) if design impedance $R_0 = 500 \Omega$ and cut-off frequency $f_c = 2000$ Hz. [6]

Or

8. (a) Explain the following in relation with filters : [6]
- (i) stop band
 - (ii) pass band
 - (iii) cut-off frequency.
- (b) A prototype high pass filter has cut-off frequency of 10 kHz and design impedance of 600Ω . Find value of L & C. Also find attenuation in dB and phase shift in degrees at frequency of 8 kHz. [6]