

Total No. of Questions—8]

[Total No. of Printed Pages—2

Seat No.	
-------------	--

[5459]-203

S.E. (IT) (I Sem.) EXAMINATION, 2018
DIGITAL ELECTRONICS AND LOGIC DESIGN
(2015 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Answer question nos. 1 or 2, 3 or 4, 5 or 6 and 7 or 8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Assume suitable data, if necessary.

1. (a) Compare TTL and CMOS logic families. [6]

(b) Minimize the given Boolean expression using Quine-McCuskey method : [6]

$$F(A, B, C, D) = \sum m(0, 1, 3, 7, 8, 9, 11, 15).$$

Or

2. (a) Convert the following numbers in Binary form : [6]

(i) $(125.12)_{10} = (?)_2$

(ii) $(337.025)_8 = (?)_2$

(iii) $(5DB.FA)_{16} = (?)_2$

(b) Implement given function using 8 : 1 MUX and logic gates. [6]

$$F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15).$$

3. (a) Design and implement T flip-flop using SR flip-flop. [6]

(b) Draw state diagram to detect sequence 101 using Moore Modeling and Mealy modeling style. [6]

P.T.O.

Or

4. (a) Give comparison of Combinational circuit with Sequential circuit. Draw and explain one-bit memory cell using NAND gates. [6]
- (b) Design sequence generator to generate sequence 1010 using shift register. [6]
5. (a) Design and implement given functions F1 and F2 using suitable PAL : [7]
- $$F1(A, B, C) = \sum m(0, 1, 3, 6, 7);$$
- $$F2(A, B, C) = \sum m(1, 2, 4, 6)$$
- (b) Write the comparison of FPGA and CPLD. [6]

Or

6. (a) Draw and explain various components used in ASM chart. [6]
- (b) Implement Full adder circuit using suitable PLA. [7]
7. (a) Explain data objects used in VHDL with appropriate examples. [6]
- (b) Write VHDL code (Entity and Architecture) for Full adder using Behavioural modeling style. [7]

Or

8. (a) Explain difference between Sequential statements and Concurrent statements used in VHDL with suitable examples. [6]
- (b) Write VHDL code for half-adder using structural modeling style. [7]