

Total No. of Questions : 10]

SEAT No. :

P3369

[Total No. of Pages : 3

[5353] - 563

TE. (Electrical)

POWER ELECTRONICS

(2015 Pattern)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to candidates:

- 1) Solve Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8, Q.9 or Q.10
- 2) Assume suitable data, if necessary.
- 3) Neat diagrams must be drawn wherever necessary..
- 4) Figures to the right indicate full marks.

Q1) a) Explain the triggering of SCR using UJT relaxation oscillator. **[5]**

- b) Draw neat circuit diagram and explain working of single phase fully controlled bridge converter feeding RL load with freewheeling diode. **[5]**

OR

Q2) a) Draw the circuit symbol and VI characteristics of GTO **[4]**

- b) Draw neat circuit diagram of a 1 phase semi controlled converter feeding R-L load at $\alpha = 90^\circ$. Draw output voltage waveform showing devices conducting during one cycle of input ac voltage **[6]**

Q3) a) Describe the principle of step up chopper. Derive an expression for the average output voltage in terms of input voltage and duty cycle. State the assumptions made. **[6]**

- b) Compare between MOSFET and BJT. **[4]**

OR

Q4) a) A step up chopper with a pulse width of 100 μ s is operating from 230 V DC Supply. Compute the average value of load voltage for a chopping frequency of 2000 Hz. **[4]**

P.T.O.

- b) For a single phase fully controlled bridge converter with R load
- i) Draw circuit diagram [2]
 - ii) Draw output voltage waveform at firing angle 60° [3]
 - iii) Write formula for average DC voltage [1]

- Q5)** a) For a 3 phase fully controlled bridge converter feeding resistive load
- i) Draw neat circuit diagram [2]
 - ii) Draw output voltage and current waveforms at $\alpha = 30^\circ$ [4]
 - iii) Write the switching sequence of SCRS clearly [2]
 - iv) Derive expression for average output voltage [2]
- b) Explain triggering of TRIAC using DIAC with neat circuit diagram [6]

OR

- Q6)** a) For a 3 phase fully controlled bridge converter feeding RL load
- i) Draw neat circuit diagram [2]
 - ii) Draw output voltage waveform at $\alpha=90^\circ$ [4]
 - iii) Write the switching sequence of SCRS clearly [2]
- b) Explain working of single phase AC voltage regulator with R Load . Draw output voltage and current waveforms. [8]

- Q7)** a) Explain with neat circuit diagram and waveforms single phase full bridge voltage source inverter with R load. [8]
- b) Compare Current Source Inverter and Voltage Source Inverter. [8]

OR

- Q8)** a) Explain sinusoidal pulse PWM technique with waveforms [8]
- b) Explain working of Current source inverter with ideal switches [8]

- Q9) a)** Explain working of three phase inverter in 180° mode of operation. For star connected load, draw output line and phase voltage waveforms. Show devices conducting in each step. [10]
- b) Draw neat diagram for Diode Clamped multilevel converter and explain its working with the help of Switching states of devices. Draw Output Phase voltage waveform. [8]

OR

- Q10)a)** State the methods for voltage control of inverters and explain any one method in detail. [8]
- b) Draw circuit diagram for three level Flying capacitor Converter and explain its principal of operation. Comment on voltage balancing of capacitors. [10]

