

Total No. of Questions—8]

[Total No. of Printed Pages—4

Seat No.	
-------------	--

**[5559]-157**


**S.E. (Electrical Engineering) (II Semester) EXAMINATION, 2019**  
**NETWORK ANALYSIS**  
**(2015 PATTERN)**

**Time : Two Hours**

**Maximum Marks : 50**


- N.B. :—** (i) Answer Q. No. 1 or 2, Q. No. 3 or 4, Q. No. 5 or 6 and Q. No. 7 or 8.  
(ii) Neat diagrams must be drawn wherever necessary.  
(iii) Figures to the right indicate full marks.  
(iv) Assume suitable data, if necessary.

1. (a) Find the mesh transformation matrix of the given circuit : [6]

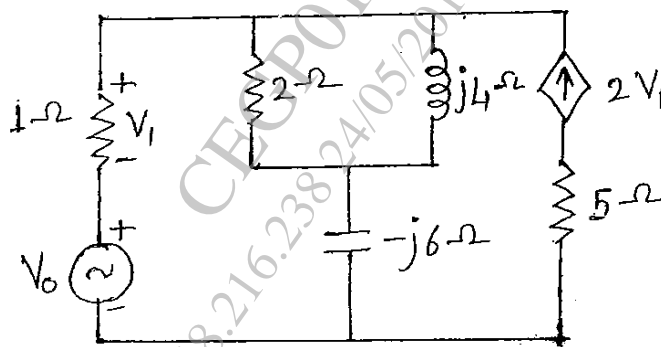

**Fig. 1(a)**

- (b) Obtain Thevenin's equivalent of the ckt shown below : [7]

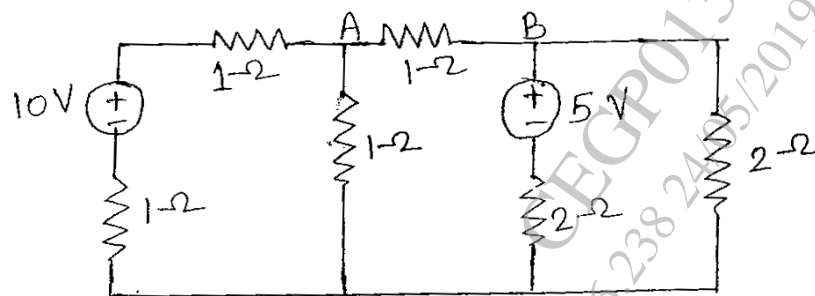

**Fig. 1(b)**

P.T.O.

Or

2. (a) Explain the concept of Duality with suitable examples. [6]  
 (b) Verify the reciprocity theorem for voltage ' $V_C$ ' and current ' $I$ ' in the network shown in fig. below : [7]

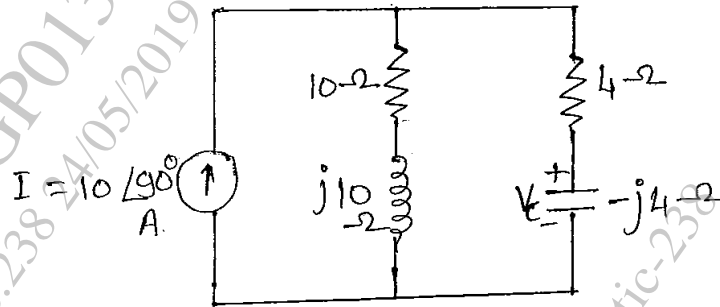


Fig. 2(b)

3. (a) RLC circuit is excited by D.C. voltage source. Find  $i(t)$  using conventional method. The switch is closed at time  $t = 0$  : [6]

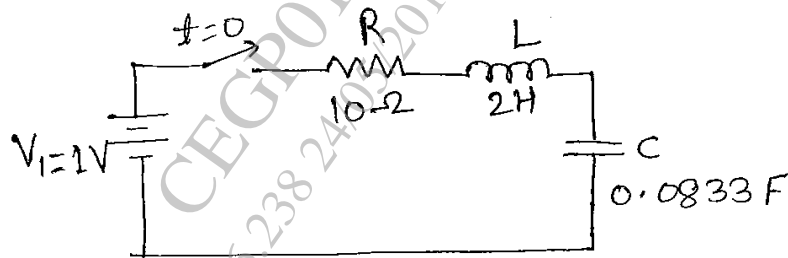


Fig. 3(a)

- (b) For the network shown in fig., find  $i(t)$  using Laplace transform with switch ' $k$ ' opened at  $t = 0$  : [6]

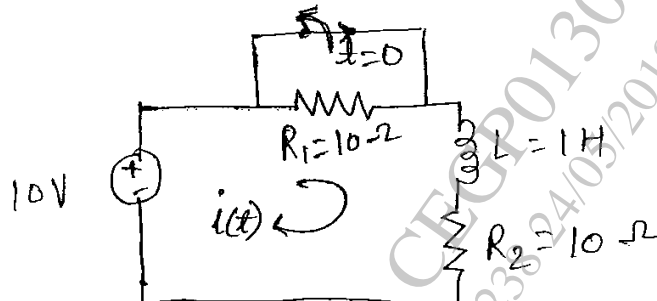


Fig. 3(b)

Or

4. (a) Find current equation when the switch is opened at  $t = 0$  : [6]

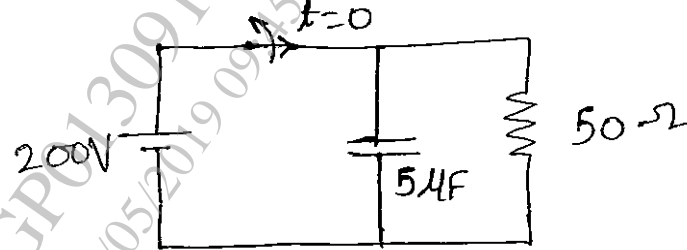


Fig. 4(a)

- (b) A series RLC ckt has a constant voltage  $V = 10$  V applied at  $t = 0$ . Using Laplace transfer find the resulting current if initial conditions are zero. [6]

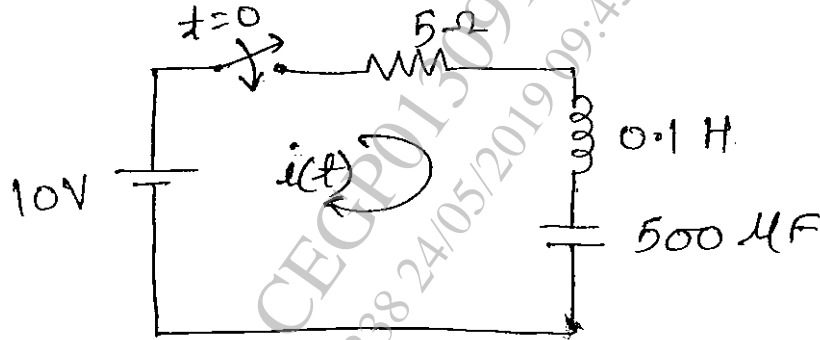


Fig. 4(b)

5. (a) Find 'h' parameters of the network shown in fig.: [7]

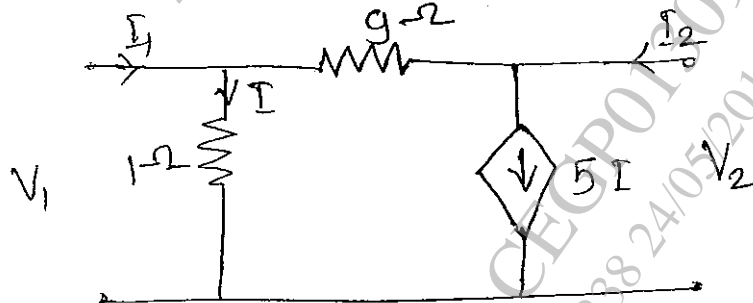


Fig. 5(a)

- (b) State the restrictions on pole zero locations for driving point function and transfer function. [6]

Or

6. (a) Derive interrelation between 'Z' and transmission parameters. [6]
- (b) For the given network function, draw pole-zero plot and obtain time domain response of voltage using graphical method : [7]

$$V(s) = \frac{5(s+5)}{(s+2)(s+7)}.$$

7. (a) What is filter ? Classify its four types and explain in detail. [6]
- (b) Design a T and  $\pi$  section constant K high pass filter having cut-off frequency of 12 kHz and nominal impedance  $R_0 = 500 \Omega$ . Also find : (i) Its characteristic impedance and phase constant at 24 kHz and (ii) attenuation at 4 kHz. [6]

Or

8. (a) Derive expression for characteristic impedance ( $Z_{0T}$  and  $Z_{0\pi}$ ), attenuation constant ( $\alpha$ ), and phase constant ( $\beta$ ) of constant K-type high pass filter from symmetrical network. [6]
- (b) Design constant K-low pass filter to have a cut-off frequency of 796 Hz when terminated in a  $600 \Omega$  resistance in both the T and  $\pi$  configurations. [6]