

Total No. of Questions—8]

[Total No. of Printed Pages—2

Seat No.	
-------------	--

**[5559]-138**

**S.E. (E&TC/Elect.) (Second Semester) EXAMINATION, 2019**

**INTEGRATED CIRCUITS**

**(2015 PATTERN)**

**Time : 2 Hours**

**Maximum Marks : 50**

**N.B. :— (i) Answer Q. 1 or Q. 2, Q. 3 or Q. 4, Q. 5 or Q. 6 and Q. 7 or Q. 8.**

**(ii) Neat diagrams must be drawn wherever necessary.**

**(iii) Figures to the right side indicate full marks.**

**(iv) Use of calculator is allowed.**

**(v) Assume suitable data if necessary.**

1. (a) Explain following OP-AMP parameters and state their ideal value [6]

i. Slew Rate. ii. Input offset current. iii. Supply voltage rejection ratio.

(b) Draw the circuit diagram of practical integrator and draw its frequency response. Write equation for output voltage  $V_o$ . [6]

Or

2. (a) Draw Block diagram of OP-AMP and explain in brief. [6]

(b) Design a practical differentiator to differentiate the input sine wave signal. Assume  $F_a=1\text{KHz}$ ,

$C_1=0.1\mu\text{f}$  and  $R_1=82\text{ Ohms}$ . [6]

3. (a) Draw circuit diagram and input-output waveform of precision half wave and full wave rectifier.

[6]

(b) Explain with a neat circuit diagram working of V to I converter with grounded load and derive

the equation for load current  $I_L$ . [6]

P.T.O.

Or

4. (a) Explain with a neat circuit diagram working of inverting Schmitt trigger with its input-output waveform and hysteresis plot. [6]

(b) Draw circuit diagram of R-2R ladder DAC and write its output voltage equation. [6]

5. (a) Explain PLL operation in detail with neat block diagram. [6]

(b) Design Wein bridge oscillator for  $F_o = 1\text{KHZ}$  and draw its circuit diagram. Assume suitable data

[7]

Or

6. (a) Draw and explain Frequency Shift Keying (FSK) demodulator using IC565. [6]

(b) . Explain with neat circuit diagram RC phase shift oscillator and write equation for frequency of oscillations  $F_o$ . [7]

7. (a) Draw circuit diagram of first order low pass butterworth filter and derive gain ( $V_o/V_{in}$ ) of filter as function of frequency. [7]

(b) Draw circuit diagram of Second order high pass butterworth filter and write its gain ( $V_o/V_{in}$ ) equation. [6]

Or

8. (a) Draw circuit diagram of first order high pass butterworth filter and derive gain ( $V_o/V_{in}$ ) of filter as function of frequency. [7]

(b) Draw circuit diagram of Second order low pass butterworth filter and write its gain ( $V_o/V_{in}$ ) equation. [6]